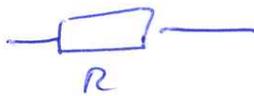


# LINEÁRNE ELEKTRONICKÉ OBVODY 1.

## OBVODY S R, L, C



$$U = RI$$

$$\frac{U}{I} = R$$




$$U = \frac{Q}{C} = \frac{1}{C} \int_{-\infty}^t I(t) dt$$



$$U = L \frac{dI}{dt}$$

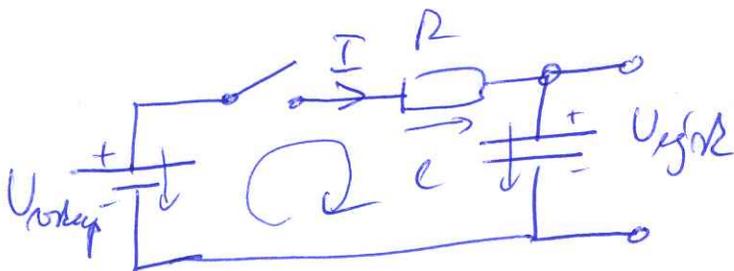Kirchoffove rovnice - poutě:  $\oint \vec{E} d\vec{l} = 0$



$$\oint \vec{E} d\vec{l} = 0 \quad -U_{\text{nap}} + RI + \frac{1}{C} \int_{-\infty}^t I dt = 0 \quad \left| \frac{d}{dt} \right.$$

$$R \frac{dI}{dt} + \frac{1}{C} I(t) = 0$$

Lineární dif.  
rovnice s konst.  
koeficienty

$$I = I_0 e^{-\frac{t}{RC}}$$

$$t=0 \Rightarrow \text{nenulový, } U_C = 0 \Rightarrow U_R = U_{\text{nap}}$$

$$I(t=0) = \frac{U_{\text{nap}}}{R}$$


$$I = \frac{U_{\text{nap}}}{R} e^{-\frac{t}{RC}}$$

# OBUODY SRLC

?

$$U_{\text{výst}} = \frac{1}{C} \int_{-\infty}^t I(t) dt = \frac{1}{C} \int_0^t \frac{U_{\text{vst}} - U/R}{R} e^{-t/RC} dt$$
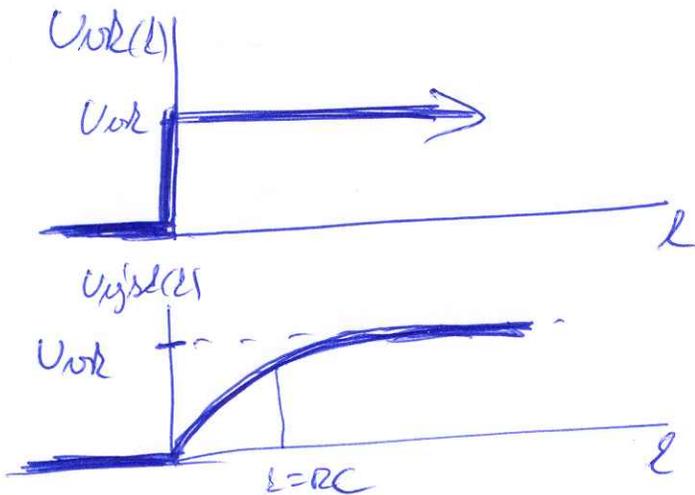
$$U_{\text{výst}} = U_{\text{vst}} \left( 1 - e^{-\frac{t}{RC}} \right)$$



Rušení diferenciálních rovnic s neprotokluní,  
 trik - komplexno-symbolická metoda:

$$\begin{aligned}
 U_{\text{vst}} &= \tilde{U}_{\text{vst}} e^{j\omega t} & \tilde{U}_{\text{vst}} & \text{- komplexní číslo} \\
 I &= \tilde{I} e^{j\omega t} & \Rightarrow U, I & \text{- komplexní veličiny} \\
 U_{\text{výst}} &= \tilde{U}_{\text{výst}} e^{j\omega t}
 \end{aligned}$$

~~Realne~~ "Realne" hodnoty komplexní  
~~veličin~~ veličin - napr. reálné části

$$\begin{aligned}
 U &= \tilde{U} e^{j\omega t} = (U_{\text{re}} + j U_{\text{im}}) e^{j\omega t} \\
 \text{Re}\{U\} &= U_{\text{re}} \cos \omega t - U_{\text{im}} \sin \omega t
 \end{aligned}$$

# OBJEKT S R, L, C

3.

Impedancia:



$$U = RI$$

$$\tilde{U} e^{j\omega t} = R \tilde{I} e^{j\omega t}$$


$$\frac{\tilde{U}}{\tilde{I}} = \boxed{Z_R = R}$$



$$U = L \frac{dI}{dt}$$

$$\tilde{U} e^{j\omega t} = L \frac{d}{dt} (\tilde{I} e^{j\omega t}) =$$
$$= L \tilde{I} j\omega e^{j\omega t}$$
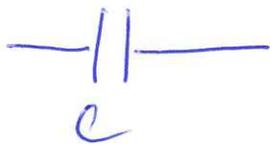
$$\frac{\tilde{U}}{\tilde{I}} = \boxed{Z_L = j\omega L}$$




$$U = \frac{1}{C} \int I dt$$

$$\tilde{U} e^{j\omega t} = \frac{1}{C} \int \tilde{I} e^{j\omega t} dt =$$
$$= \frac{1}{C} \tilde{I} \frac{e^{j\omega t}}{j\omega}$$

$$\frac{\tilde{U}}{\tilde{I}} = \boxed{Z_C = \frac{1}{j\omega C}}$$

# OBVODY SR, L, C

4.

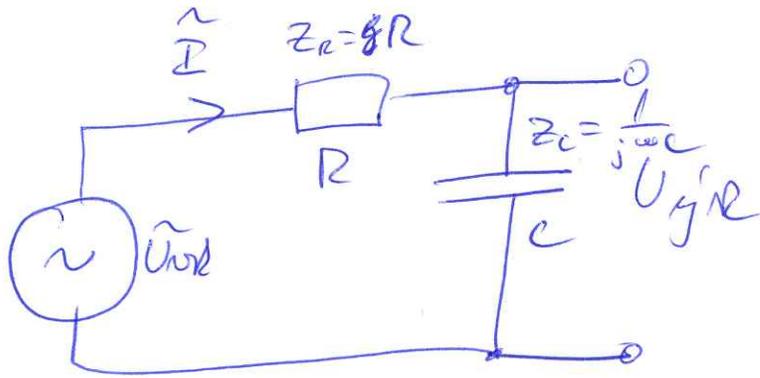

$$\tilde{I} = \frac{\tilde{U}_{0sk}}{R + \frac{1}{j\omega C}}$$


$$\tilde{U}_{1sk} = \frac{1}{j\omega C} \cdot \tilde{I} = \frac{1}{R + \frac{1}{j\omega C}} \tilde{U}_{0sk}$$

$$\tilde{U}_{1sk} = \frac{1}{1 + j\omega RC} \tilde{U}_{0sk}$$

úroveň medzi  $\tilde{U}_{0sk}$  a  $\tilde{U}_{1sk}$

1. Podiel amplitúd

$$\frac{|U_{1sk}|}{|U_{0sk}|} = \left| \frac{1}{1 + j\omega RC} \right| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

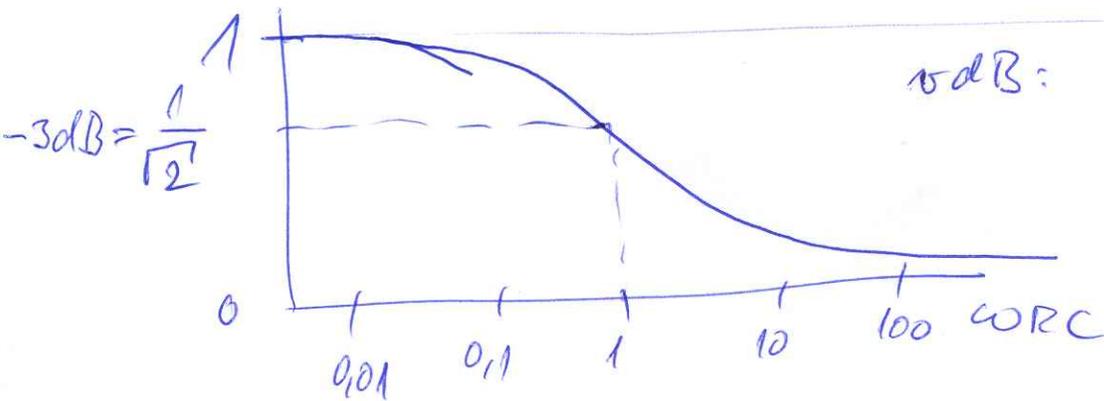

$$\text{dB: } 20 \log \frac{|U_{1sk}|}{|U_{0sk}|} = -3 \text{ dB}$$

Oboody A P, L, C

5.

2. Faza medru  $U_{nr}$  a  $U_{jnr}$

$$\tan \varphi = \frac{\operatorname{Im} \left\{ \frac{U_{jnr}}{U_{nr}} \right\}}{\operatorname{Re} \left\{ \frac{U_{jnr}}{U_{nr}} \right\}}$$

$$\tan \varphi = -\omega RC$$

